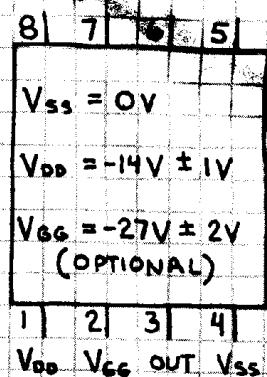



# NOISE GENERATOR

## S2688 / MM5837N

PRODUCES BROADBAND WHITE NOISE FOR AUDIO AND OTHER APPLICATIONS. THE NOISE QUALITY IS VERY UNIFORM. IT IS PRODUCED BY A 17-BIT SHIFT REGISTER WHICH IS CLOCKED BY AN INTERNAL OSCILLATOR.




### WHITE NOISE SOURCE

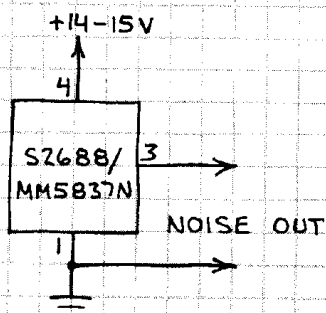


CONNECT OUTPUT TO AUDIO AMPLIFIER TO HEAR NOISE. USE 7815 VOLTAGE REGULATOR TO OBTAIN  $+15$  VOLTS.

### PINK NOISE SOURCE

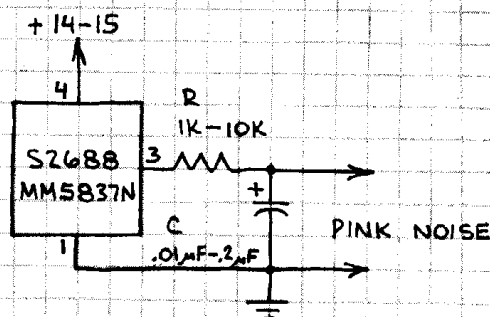


CHANGE  $R$  AND  $C$  TO ALTER NOISE SPECTRUM. ALSO, TRY LOWER SUPPLY VOLTAGES TO CHANGE SPECTRUM.

### COIN TOSSER

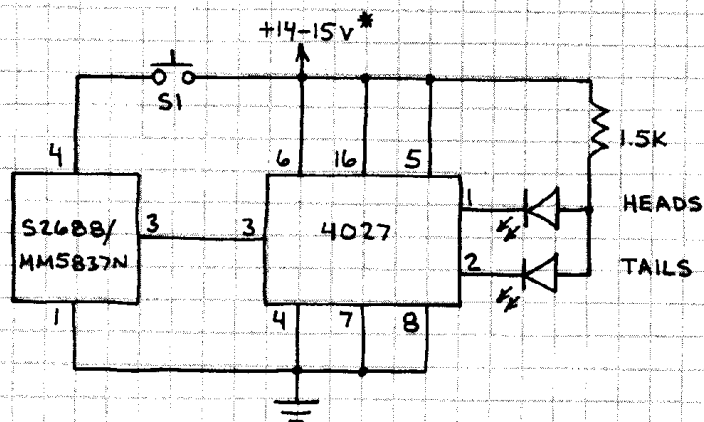

PRESS  $S1$ ; BOTH LEDs GLOW. RELEASE  $S1$  AND ONLY ONE GLOWS. GROUND INPUTS OF UNUSED HALF OF 4027 (PINS 9, 10, 11, 12 AND 13). \* (OK TO USE 9-VOLT BATTERY AS POWER SUPPLY.)

### SNARE / BRUSH NOISE

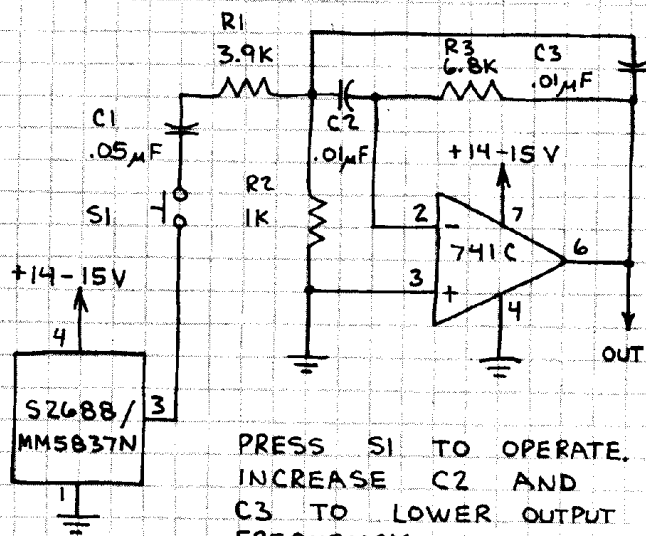

PRESS  $S1$  TO OPERATE. INCREASE  $C2$  AND  $C3$  TO LOWER OUTPUT FREQUENCY.

# Build a PINK NOISE GENERATOR for AUDIO TESTING

*Uses a new MOS noise generator IC.*

BY DENNIS BOHN

**A**N INCREASING number of audio-philosophers are incorporating graphic equalizers into their hi-fi music systems. The new component is most often used as a "super" tone control that offers a degree of frequency response compensation beyond the capabilities of bass and treble controls. However, adjusting 10 to 30 controls to compensate for acoustic deficiencies in the listening room can be challenging. This project—a pink noise generator—makes the job a little easier. It provides a reference signal for performing equalizer adjustments, and uses just one IC and a few passive components.

The IC, National Semiconductor's MM5837, is a digital pseudo-random sequence generator which will produce a broadband white noise signal for audio applications that's converted to pink noise by a passive filter. Unlike traditional semiconductor junction noise sources, the MM5837 provides uniform noise quality and output amplitude. Although it was originally developed with electronic organs and synthesizers in mind, it is equally suited to room equalization applications. A block diagram of the MM5837 is shown in Fig. 1.

**White vs. Pink Noise.** The output of the MM5837 is broadband white noise. Since pink noise is used in most audio work, it is helpful to understand the difference between the two.

White noise is a composite signal with contributions from all frequencies and a spectral density substantially independent of frequency (equal energy per constant bandwidth). It is characterized by a 3-dB increase in amplitude per octave of frequency change. In comparison, pink noise has a flat amplitude response per octave of frequency (equal energy per octave). Pink noise allows correlation between successive octave equalizer stages by insuring that the same amplitude of input signal is used for each as a reference.

The network required to convert white noise to pink noise is simply a -3-dB/octave low-pass filter; but it presents an interesting problem in circuit design. If capacitive reactance (and thus the response of a simple RC or first-order filter) varies at a rate of -6 dB/octave, how can a slope of less than -6 dB/

octave be obtained? The solution lies in cascading several stages of lag compensation so that the zeros of one stage partially cancel the poles of the next stage. Such a network, shown in Fig. 2, has a -3-dB/octave characteristic ( $\pm 1/4$  dB) from 10 to 40,000 Hz.

The complete pink noise generator in Fig. 3 gives a flat spectral distribution (per octave) over the audio band from 20 to 20,000 Hz. An 11.5-V p-p random pulse train appears at pin 3 of the IC, and is attenuated by the filter. The actual output across C5 is about 1 V p-p ac of pink noise riding on an 8.5-V dc level.

**Construction.** Since the circuit is fairly simple, it can be constructed on a small circuit board using printed circuit, point-to-point wiring, or Wire-Wrap techniques. Resistors in the filter network should have close tolerances. Premium-grade tantalum and polystyrene, ceramic, and film capacitors are recommended. Observe standard precautions in handling the MOS device, and use an IC socket or Molex Soldercons. ◇

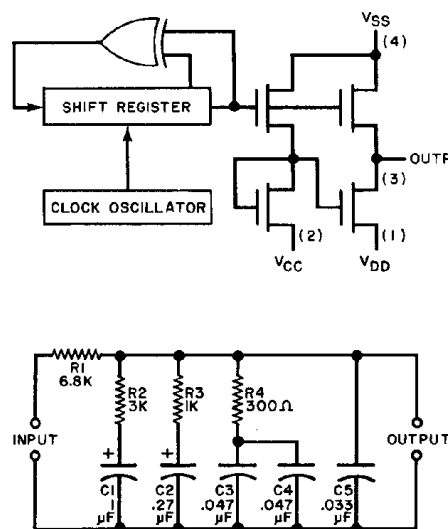


Fig. 1. Block diagram of the MM5837 noise source.

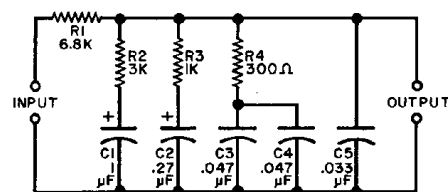


Fig. 2. Low-pass filter with -3-dB/octave response.

## PARTS LIST

- C1—1-μF, 35-V tantalum capacitor
- C2—0.27-μF, 35-V tantalum capacitor
- C3, C4—0.047-μF capacitor
- C5—0.033-μF capacitor
- C6—100-μF, 35-V electrolytic capacitor
- IC4—MM5837 noise generator IC
- R1—6800-ohm, 1/4-W, 5% resistor
- R2—3000-ohm, 1/4-W, 5% resistor
- R3—1000-ohm, 1/4-W, 5% resistor
- R4—300-ohm, 1/4-W, 5% resistor
- Misc.—Circuit board, 15-volt regulated supply, output jack, output connector, IC socket or Molex Soldercons, hookup wire, solder, suitable enclosure, etc.

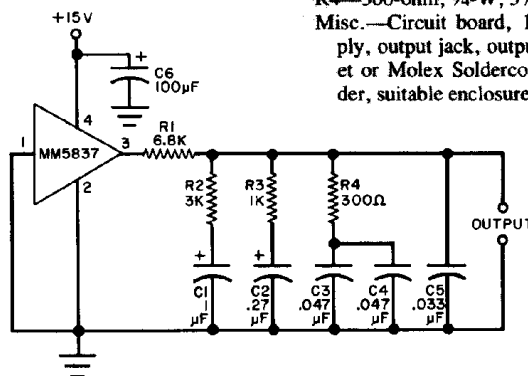


Fig. 3. Schematic diagram of the pink noise generator.